 


# VLSI Physical Design with Timing Analysis

## Assignment - 3

**Qns 1:** Consider the following circuit.



Delay values of Flipflop and Combinational circuit are:  $t_{\text{setup}} = 3\text{ns}$  and  $t_{\text{hold}} = 2\text{ns}$ . The delay of the buffer is  $t_{\text{buf}} = 2\text{ns}$ .

Delay	$t_{\text{clk-q}}$	$t_{\text{NAND3}}$	$t_{\text{NOT}}$	$t_{\text{NOR}}$	$t_{\text{NAND2}}$
Max	3 ns	2.5 ns	1 ns	2.5 ns	2 ns
Min	2 ns	1.5 ns	0.3 ns	1.5ns	1.2 ns

The maximum frequency at which the given circuit can operate without failure is \_\_\_ (MHz)  
(Rounded to 2 decimal points)


**Ans:** 90.90 MHz

**Qns 2:** Choose the correct hold constraint equation for the circuit given in question 1.

 - a.  $4\text{ns} - 2\text{ns} \leq 2\text{ns} + 3\text{ns}$
- b.  $4\text{ns} \leq 2\text{ns} + 3\text{ns}$
- c.  $4\text{ns} \leq 3\text{ns} + 5.5\text{ns}$
- d.  $4\text{ns} - 2\text{ns} \leq 3\text{ns} + 5.5\text{ns}$

**Ans:** (b)

**Qns 3 :** Consider the following circuit.




Delay values of Flipflop and Combinational circuit are:  $t_{\text{setup}} = 3\text{ns}$  and  $t_{\text{hold}} = 2\text{ns}$ . The delay of the buffer is  $t_{\text{buf}} = 2\text{ns}$ .

Delay	$t_{\text{clk-q}}$	$t_{\text{NAND3}}$	$t_{\text{NOT}}$	$t_{\text{NOR}}$	$t_{\text{NAND2}}$
Max	3 ns	2.5 ns	1 ns	2.5 ns	2 ns
Min	2 ns	1.5 ns	0.3 ns	1.5 ns	1.2 ns

The maximum frequency at which the given circuit can operate without failure is\_\_\_\_(MHz)  
(Rounded to 2 decimal points)

 **Ans: 66.67 MHz**

**Qns 4:** Consider the following circuit.



Delay values of Flipflop and Combinational circuit are:  $t_{\text{setup}} = 3\text{ns}$  and  $t_{\text{hold}} = 2\text{ns}$ . The clock period is  $T_{\text{CLK}} = 20\text{ns}$ .


Delay	$t_{\text{clk-q}}$	$t_{\text{NAND3}}$	$t_{\text{NOT}}$	$t_{\text{NOR}}$	$t_{\text{NAND2}}$
Max	3 ns	2.5 ns	1 ns	2.5 ns	2 ns
Min	2 ns	1.5 ns	0.3 ns	1.5 ns	1.2 ns

What is the maximum allowable jitter ( $t_{\text{jitter}}$ ) in the clock signal so that the given circuit works at the given frequency without failure?

- 0.5 ns
- 1.5 ns
- 2.5 ns
- 3.5 ns

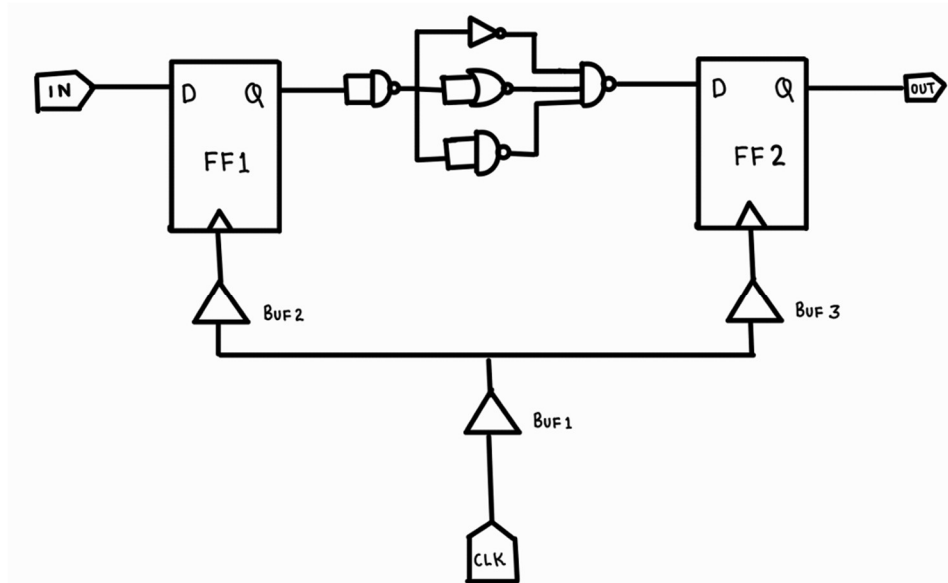**Ans: (b)**

**Qns 5 :** Consider the following circuit.



Delay	$t_{clk-q}(FF_1)$	$t_{clk-q}(FF_2)$	$t_{NAND3}$	$t_{NOT}$	$t_{NOR}$	$t_{NAND2}$
Max	3.8 ns	5 ns	2.5 ns	1 ns	2.5 ns	2 ns
Min	2 ns	2.8 ns	1.5 ns	0.3 ns	1.5 ns	1.2 ns

The delays of buffers  $t_{buf1} = 1.2\text{ns}$ ,  $t_{buf2} = 0.9\text{ns}$ , and  $t_{buf3} = 0.7\text{ns}$ . The setup and hold time of both flipflops is  $t_{setup} = 2\text{ns}$  and  $t_{hold} = 1\text{ns}$  respectively.

The On-chip variation is modeled as

set\_timing\_derate -early 0.9

set\_timing\_derate -late 1.12

set\_timing\_derate -late 1.08 -cell\_check

With On-chip variation, the maximum frequency at which the given circuit can operate without failure is \_\_\_\_ (MHz) (Rounded to 2 decimal points)


**Ans: 67.12 MHz**

**Qns 6 :** The value of common path pessimism (CPP) in the circuit given in question 5 is \_\_\_\_ps

**Ans: 264 ps**

**Qns 7 to 9: Question Label: Comprehension**

Consider the following logic circuit.

 

Logic gate	Rise delay(ns)	Fall delay(ns)
NAND	4	3
NOR	3	5
AND	2	3
OR	5	4
Buffer	1	2

Arrival Time at all primary inputs A, B, C, D and E is 0/0.

Required Time at node 'N' is 16/13

**Qns 7:** The fall output arrival time at node 'J' is \_\_\_\_ (ns)

**Ans:** 6 ns

**Qns 8:** The rise input required time at node 'G' in the given circuit is \_\_\_\_ (ns)

**Ans:** -3 ns

**Qns 9:** The slack(rise/fall) at node 'H' in the given circuit is \_\_\_\_

- a. 7/2
- b. 7/-4
- c. 0/-4
- d. 7/-4

**Ans:** (c)

**Qns 10:** Choose the incorrect option(s) about clock skew and clock jitter.

- a. Excessive skew can cause timing violations (setup or hold violations) leading to functional errors.
- b. Clock skew is non-deterministic in nature while Clock Jitter is deterministic in nature.
- c. Clock skew occurs due to noise & instability in clock while clock jitter occurs due to physical layout & propagation delay.
- d. Clock jitter can lead to data corruption in high-speed designs.

**Ans:** (b, c)

## SOLUTION

### Sol 1.

The max. timing constraint for positive skew is

$$T_{CLK} \geq t_{CLK-q}^{max} + t_{comb.}^{max} + t_{setup} - t_{buf}$$

$$t_{comb}^{max} = t_{critical} = t_{NAND2}^{max} + t_{NOR}^{max} + t_{NAND3}^{max}$$
$$t_{comb.}^{max} = 2 + 2.5 + 2.5 = 7ns$$

$$T_{CLK} \geq 3 + 7 + 3 - 2$$

$$T_{CLK} \geq 11ns$$

$$\text{max. frequency } f_{max} = \frac{1}{T_{CLK}^{min.}}$$

$$f_{max} = \frac{1}{11 \times 10^{-9}}$$

$$f_{max} = 90.9 \text{ MHz}$$

### Sol 2.

Hold timing constraint (min. timing constraint) equation for positive skew:

$$t_{hold} + t_{buf} \leq t_{CLK-q}^{min.} + t_{comb}^{min.}$$

$$t_{comb}^{min.} = t_{NAND2}^{min.} + t_{NOR}^{min.} + t_{NAND3}^{min.}$$

$$t_{comb}^{min.} = 1.2 + 0.3 + 1.5$$

$$t_{comb}^{min.} = 3ns$$

$$\text{now, } 2ns + 2ns \leq 2ns + 3ns$$

$$\text{or } 4ns \leq 2ns + 3ns$$

**Sol 3.**

In this case, max-timing constraint equation:

$$T_{CLK} \geq t_{CLK-q}^{max} + t_{comb}^{max} + t_{setup} + t_{buf}$$

$$t_{comb}^{max} = 7 \text{ ns} \quad (\text{calculated in solution of Q.1})$$

$$T_{CLK} \geq 3 + 7 + 3 + 2$$

$$T_{CLK} \geq 15 \text{ ns}$$

$$f_{max} = \frac{1}{T_{CLK}^{min}} = \frac{1}{15 \text{ n}}$$

$$f_{max} = 66.67 \text{ MHz}$$

**Sol 4.**

Case I: Max. timing analysis considering clock jitter:

$$T_{CLK} \geq t_{CLK-q}^{max} + t_{comb}^{max} + t_{setup} + 2 t_{jitter}$$

↳ calculated in solution of Q.1

$$20 \geq 3 + 7 + 3 + 2 t_{jitter}$$

$$t_{jitter} \leq 3.5 \text{ ns}$$

Case II: min. timing analysis considering clock jitter:

$$t_{hold} \leq t_{CLK-q}^{min} + t_{comb}^{min} - 2 t_{jitter}$$

↳ calculated in solution of Q.2

$$2 \leq 2 + 3 - 2 t_{jitter}$$

$$t_{jitter} \geq 1.5 \text{ ns}$$

Now. max. allowable jitter,  $t_{jitter} = \min. (3.5 \text{ ns}, 1.5 \text{ ns})$

$$t_{jitter} = 1.5 \text{ ns}$$

Sol 5.

$$\text{capture clock path} = 1.2 + 0.7 = 1.9 \text{ ns}$$

$$\text{Launch clock path} = 1.2 + 0.9 = 2.1 \text{ ns}$$

$$\text{max. data path} = t_{\text{CLK-Q}}^{\text{max}} + t_{\text{comb}}^{\text{max}}$$

calculated in solution of Q.1

$$\text{max. data path} = 3.8 + 7 = 10.8 \text{ ns}$$

With OCV:

$$T_{\text{CLK}} + [\text{capture clock path}] * (0.9) - t_{\text{setup}} * (1.08) \geq (\text{Launch clock path} + \text{max. data path}) * (1.12)$$

$$T_{\text{CLK}} + 1.9 * 0.9 - 2 * 1.08 \geq (2.1 + 10.8) * 1.12$$

$$T_{\text{CLK}} + 1.71 - 2.16 \geq 14.448$$

$$T_{\text{CLK}} \geq 14.898 \text{ ns}$$

$$f_{\text{max}} = \frac{1}{14.898 \text{ n}}$$

$$f_{\text{max}} = 67.12 \text{ MHz}$$

Sol 6.

CPP = Latest AT @ common point - earliest AT @ common point

$$\text{CPP} = 1.2 * 1.12 - 1.2 * 0.9$$


$$\text{CPP} = 0.264 \text{ ns}$$

$$\text{CPP} = 264 \text{ ps}$$

**Sol 7-9.**

Equations used in the solution:

For inverting gates:	For non inverting gates:
output rise AT = max(input fall AT) + trise	output rise AT = max(input rise AT) + trise
output fall AT = max(input rise AT) + tfall	output fall AT = max(input fall AT) + tfall
input rise RT = min(output fall RT) – tfall	input rise RT = min(output rise RT) – trise
input fall RT = min(output rise RT) – trise	input fall RT = min(output fall RT) – tfall

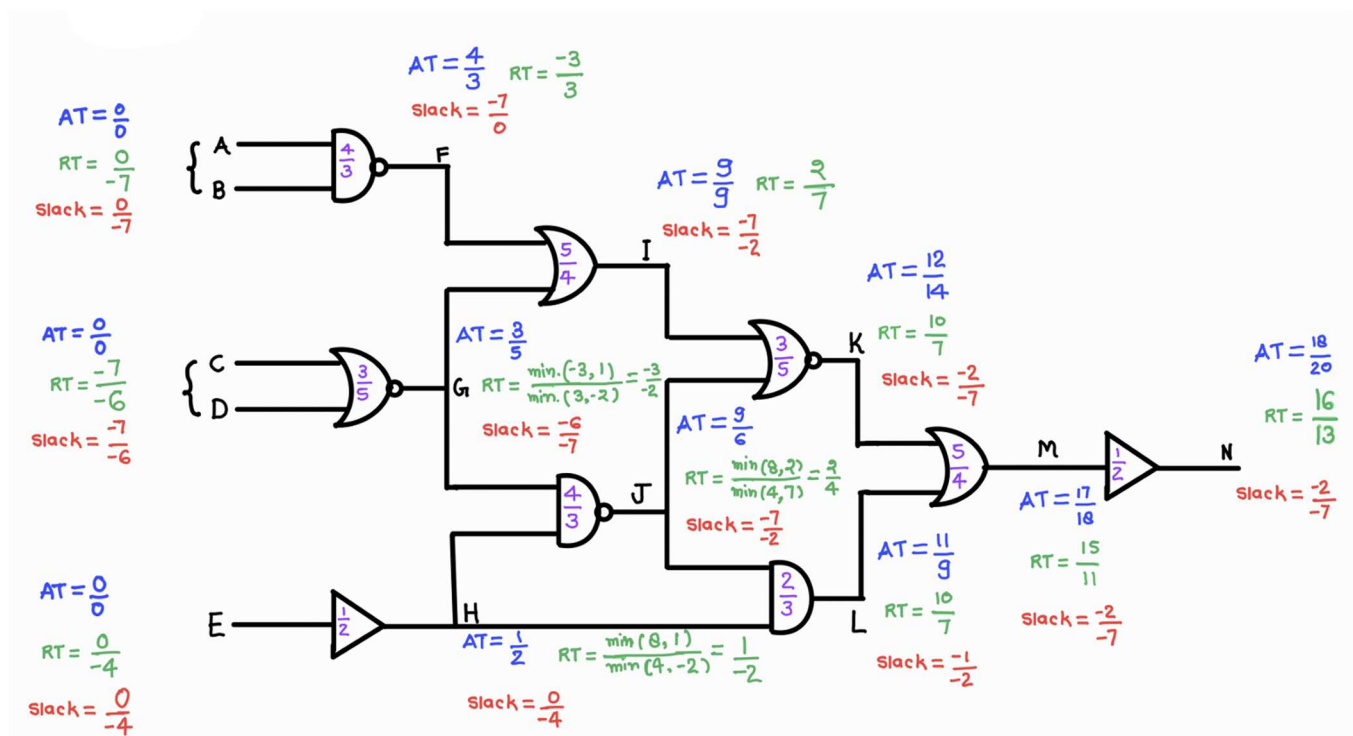**Sol 10.** Refer lecture notes