



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

VLSI Physical Design with Timing Analysis

Lecture – 9: Delay Parameters of Combinational Circuits

Bishnu Prasad Das

Department of Electronics and Communication Engineering




Contents

- Combinational Circuits
- Delay Parameters of Logic gate
(1) Propagation Delay and (2) Transition time
- Delay of Timing path




Combinational Circuits

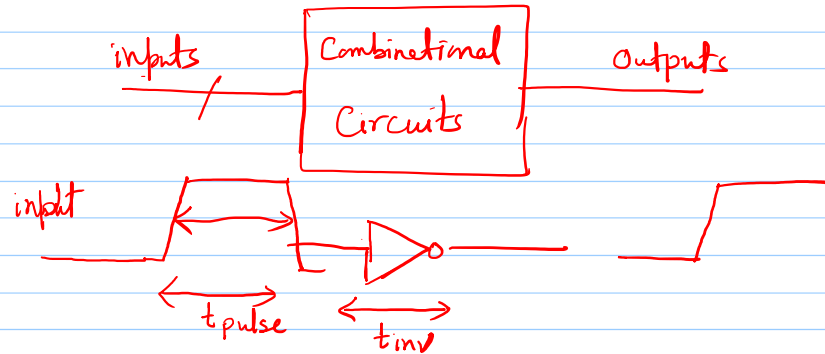

Case I $t_{\text{pulse}} > t_{\text{inv}}$, then the pulse will appear at the output of the gate

Case II $t_{\text{pulse}} < t_{\text{inv}}$, then the pulse will not appear at the output


 
This property of the logic gate is called
inertial delay property



Propagation Delay of Combinational Circuits :

of logic gate

 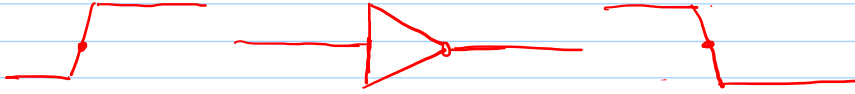- It is measured between the 50% transition points of the input and output waveforms.



Types of Propagation Delay

t_{rise}

- **Rise Propagation Delay (T_{plh})** = The signal-delay time between 50% of the input and 50% of the output when the output changes from low to high level.


output signal

(t_{fall})



- **Fall Propagation Delay (T_{phl})** = The signal-delay time between 50% of the input and 50% of the output when the output changes from high to low level.

output signal


 
- **Average propagation delay** $t_p = (T_{phl} + T_{plh})/2$



Inverting gate

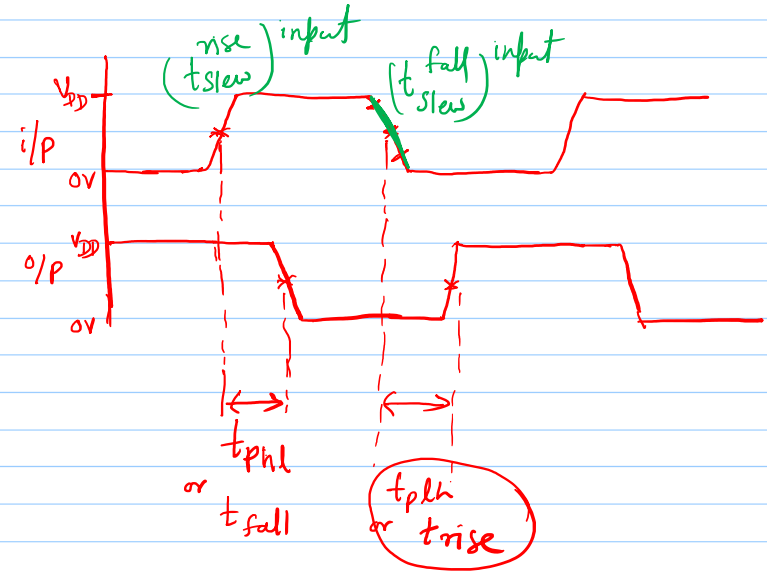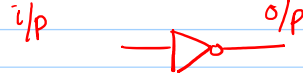

Non-inverting gate

 
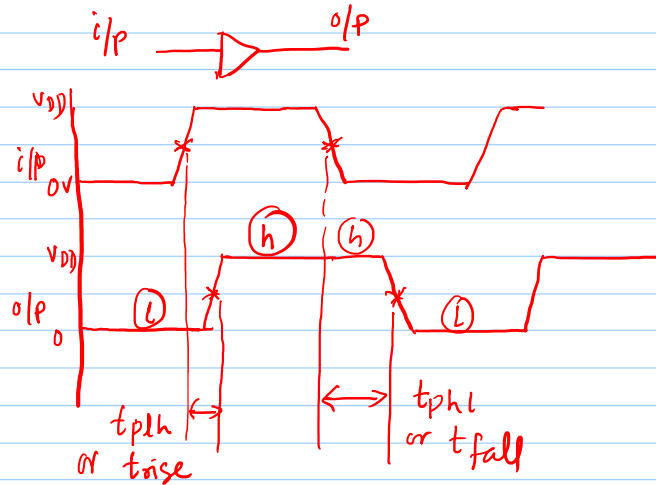



Rise transition delay

- The time taken by the signal to rise from 10% (20%) to 90% (80%) of its maximum value.

Fall transition delay

 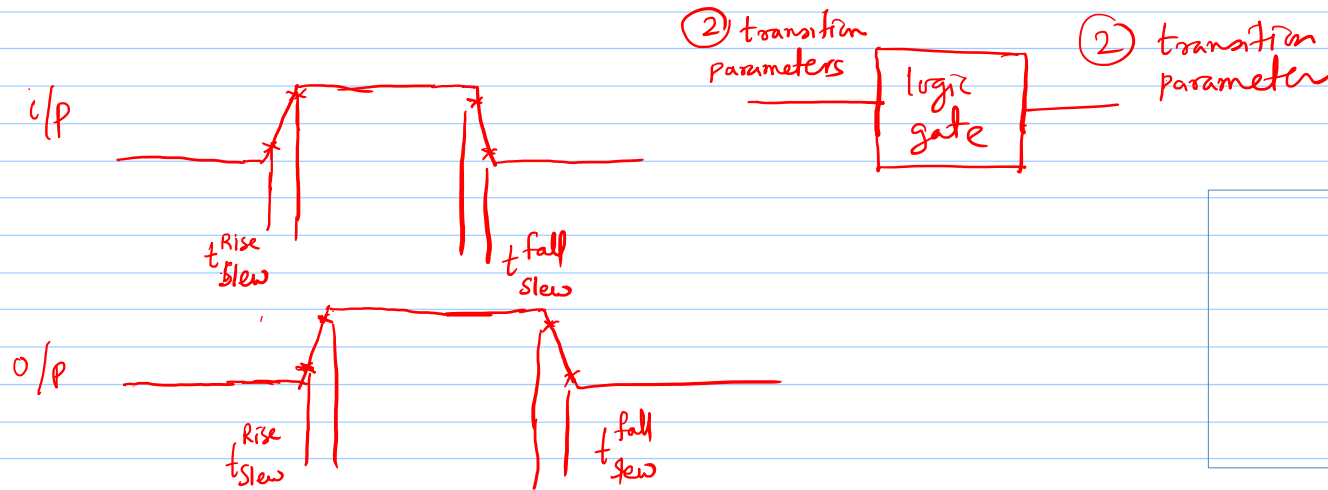- The time taken by the signal to fall from 90% (80%) to 10% (20%) of its maximum value.



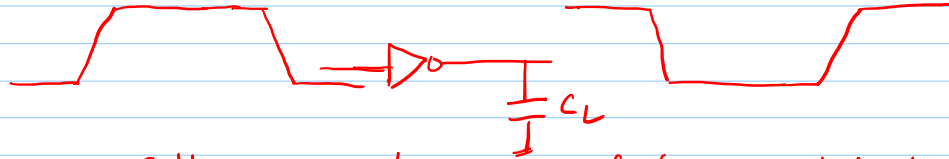


$$\begin{aligned} \text{Cell rise or } t_{plh} &= f(C_L, \text{input transition time}) \\ &= f(C_L, \text{input fall transition time}) \end{aligned}$$


$$\text{Cell fall or } t_{phl} = f(C_L, \text{input rise transition time})$$


$$\text{Output transition time (Rise)} = f(C_L, \text{input fall transition time})$$
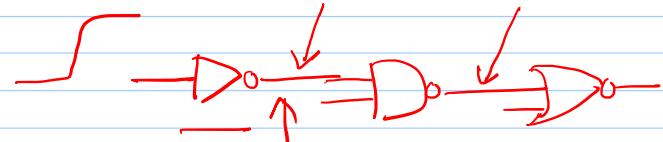
$$\text{Output transition time (Fall)} = f(C_L, \text{input rise transition time})$$



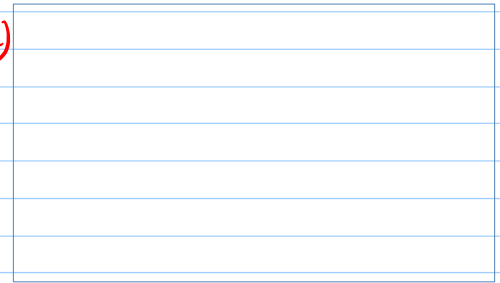- ① Cell rise
- ② Cell fall
- ③ Output transition time (Rise)
- ④ output transition time (fall)



 

```

pin (OUT) {
  max_transition : 1.0;
  timing() {
    related_pin : "INP1";
    timing_sense : negative_unate;
    ① cell_rise(delay_template_3x3) {
      index_1 ("0.1, 0.3, 0.7"); /* Input transition */
      index_2 ("0.16, 0.35, 1.43"); /* Output capacitance */
      values ( /* 0.16      0.35      1.43 */ \
        /* 0.1 */  "0.0513, 0.1537, 0.5280", \
        /* 0.3 */  "0.1018, 0.2327, 0.6476", \
        /* 0.7 */  "0.1334, 0.2973, 0.7252");
    }
    ② cell_fall(delay_template_3x3) {
      index_1 ("0.1, 0.3, 0.7"); /* Input transition */
      index_2 ("0.16, 0.35, 1.43"); /* Output capacitance */
      values ( /* 0.16      0.35      1.43 */ \
        /* 0.1 */  "0.0617, 0.1537, 0.5280", \
        /* 0.3 */  "0.0918, 0.2027, 0.5676", \
        /* 0.7 */  "0.1034, 0.2273, 0.6452");
    }
  }
}

```

t_{ph} or t_{rise}

lib → used extensively in STA

t_{ph} or t_{fall}

```


pin (OUT) {
  max_transition : 1.0;
  timing() {
    related_pin : "INP";
    timing_sense : negative_unate;
    3) rise_transition(delay_template_3x3) {
      index_1 ("0.1, 0.3, 0.7"); /* Input transition */
      index_2 ("0.16, 0.35, 1.43"); /* Output capacitance */
      values ( /* 0.16      0.35      1.43 */ \
        /* 0.1 */ "0.0417, 0.1337, 0.4680", \
        /* 0.3 */ "0.0718, 0.1827, 0.5676", \
        /* 0.7 */ "0.1034, 0.2173, 0.6452");
    }
    4) fall_transition(delay_template_3x3) {
      index_1 ("0.1, 0.3, 0.7"); /* Input transition */
      index_2 ("0.16, 0.35, 1.43"); /* Output capacitance */
      values ( /* 0.16      0.35      1.43 */ \
        /* 0.1 */ "0.0817, 0.1937, 0.7280", \
        /* 0.3 */ "0.1018, 0.2327, 0.7676", \
        /* 0.7 */ "0.1334, 0.2973, 0.8452");
    }
  }
}

```

Output Signal Rise transition

Output signal fall transition.

Delay of a timing Path

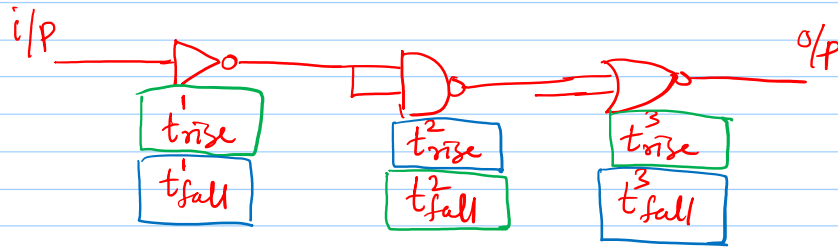


$$\begin{array}{lcl} t_{rise}^1 = 2 & \rightarrow & t_{rise}^2 = 4 \\ t_{fall}^1 = 3 & \rightarrow & t_{fall}^2 = 4 \end{array}$$
$$\begin{array}{lcl} t_{rise}^2 = 4 & \rightarrow & t_{rise}^3 = 6 \\ t_{fall}^2 = 4 & \rightarrow & t_{fall}^3 = 3 \end{array}$$


$$T_{rise} = 2 + 4 + 6 = 12$$


$$T_{fall} = 3 + 4 + 3 = 10$$


$$T_{rise} > T_{fall}$$
 
$$T_{rise} = (t_{plh})^{Path} = t_{rise}^1 + t_{fall}^2 + t_{rise}^3$$
$$T_{fall} = (t_{phl})^{Path} = t_{fall}^1 + t_{rise}^2 + t_{fall}^3$$



 

 

 

Thank You

