



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# VLSI Physical Design with Timing Analysis

## Lecture – 8: Timing Arcs and Unateness

Bishnu Prasad Das

Department of Electronics and Communication Engineering





# Contents

- Definition of Timing arcs
- Source Pin and Sink pin
- Unatenesss
  - (1) Positive Unate,
  - (2) Negative Unate
  - (3) Non-Unate
- Use of Unateness



 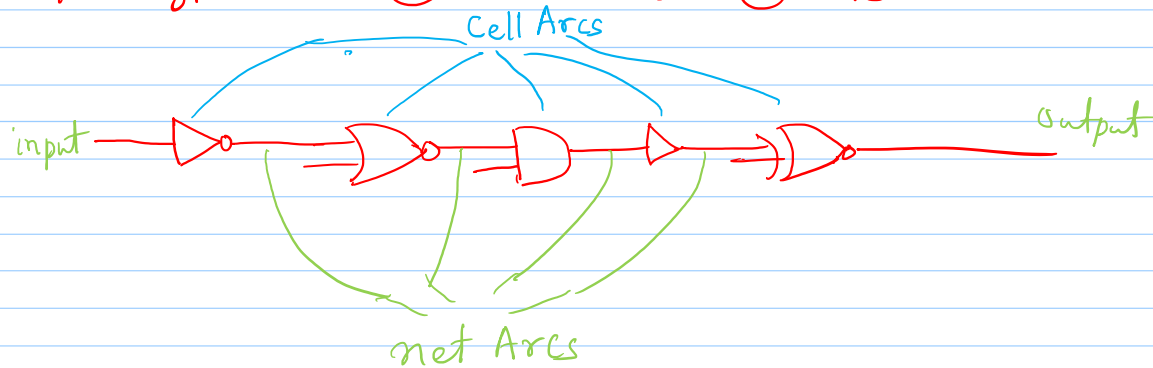
## Timing Arcs

- It is defined as the relationship between 2-pins of a logic gate
- It is useful for the STA tools to do timing analysis
- It is basically a part of the timing path
- Two types - (1) cell Arcs (2) net Arcs



## Source Pin and Sink Pin

 


For gate  $G_1$ , B and C are source pin and  $O_2$  is the sink pin

For gate  $G_2$ , A and  $O_2$  are source pin and  $O_1$  is the sink pin

In case of cell Arcs: input pins <sup>of cell</sup> are source pin  
output pins <sup>of cell</sup> are sink pin

 In case of net Arcs: output pin of cell are source pin  
input pin of the cells are sink pin



## Unateness

Each timing Arcs has a timing sense.





Change in the output transition w.r.t input transition.

### (1) Positive Unate







input signal is "Rising" → Output signal is "rising" or No change.  
" " is "falling" → " " " " "falling" or No change

Bubbles

  

## AND gate

AND gate has 4 timing Arcs

      


## (2) Negative Unate


input signal is "rising"  $\rightarrow$  output signal is "falling" or no change

input " " "falling"  $\rightarrow$  " " is "rising" or no change






### (i) Inverter

 

2 timing Arcs

 

(ii) 2-input NAND gate

     


4 timing Arcs






## Non-Unate gate

### XOR gate

 


Positive unate  
if  $A=0$

 

Negative unate  
if  $A=1$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

 

```

pin (OUT) {
  max_transition : 1.0;
  timing() {
    related_pin : "INP";
    timing_sense : negative_unate;
    rise_transition(delay_template_3x3) {
      index_1 ("0.1, 0.3, 0.7"); /* Input transition */
      index_2 ("0.16, 0.35, 1.43"); /* Output capacitance */
      values ( /* 0.16 0.35 1.43 */ \
        /* 0.1 */ "0.0417, 0.1337, 0.4680", \
        /* 0.3 */ "0.0718, 0.1827, 0.5676", \
        /* 0.7 */ "0.1034, 0.2173, 0.6452");
    }
    fall_transition(delay_template_3x3) {
      index_1 ("0.1, 0.3, 0.7"); /* Input transition */
      index_2 ("0.16, 0.35, 1.43"); /* Output capacitance */
      values ( /* 0.16 0.35 1.43 */ \
        /* 0.1 */ "0.0817, 0.1937, 0.7280", \
        /* 0.3 */ "0.1018, 0.2327, 0.7676", \
        /* 0.7 */ "0.1334, 0.2973, 0.8452");
    }
  }
}

```

Source : Static Timing Analysis For Nanometer Designs: A Practical Approach by J. Bhasker and Rakesh Chadha




## Timing Arcs of Sequential Circuits

(1) For Synchronous inputs

- (i) Setup check Arc (Rising and falling)
- (ii) Hold check Arc (Rising and falling)


(2) For asynchronous inputs (Reset)



 
- (i) Recovery check arc
- (ii) Removal check arc



(3) For Synchronous outputs ( $Q$ , and  $\bar{Q}$ )



 
- (i) Clock-to-output propagation delay (rising and falling)



   


Reset



$\text{Reset} = 1 \Rightarrow Q = 0$

   

## Recovery check Arc

 

## Removal check Arc

  

```
pin (D) {  
    direction : input;  
    ...  
    timing () {  
        related_pin : "CK";  
        timing_type : "setup_rising";  
        rise_constraint ("setuphold_template_3x3") {  
            index_1("0.4, 0.57, 0.84"); /* Data transition */  
            index_2("0.4, 0.57, 0.84"); /* Clock transition */  
            values( /*      0.4      0.57      0.84 */ \  
                /* 0.4 */ "0.063, 0.093, 0.112", \  
                /* 0.57 */ "0.526, 0.644, 0.824", \  
                /* 0.84 */ "0.720, 0.839, 0.930");  
        }  
    }  
}
```

Source : Static Timing Analysis For Nanometer Designs: A Practical Approach by J. Bhasker and Rakesh Chadha

# Thank You

