



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

VLSI Physical Design with Timing Analysis

Lecture – 18: STA for Combinational Circuits – II

Bishnu Prasad Das

Department of Electronics and Communication Engineering



Contents

- Critical Path finding



Inverting type of gates



① Output rise A.T. = $\max(\text{input fall A.T.}) + \text{Rise delay}$


② Output fall A.T. = $\max(\text{input rise A.T.}) + \text{fall delay}$

③ input rise A.T. =

input rise R.T. = $\min(\text{output fall R.T.}) - \text{fall delay}$


④ input fall A.T.

 input fall R.T. = $\min(\text{output rise A.T.}) - \text{rise delay}$



Ex:1

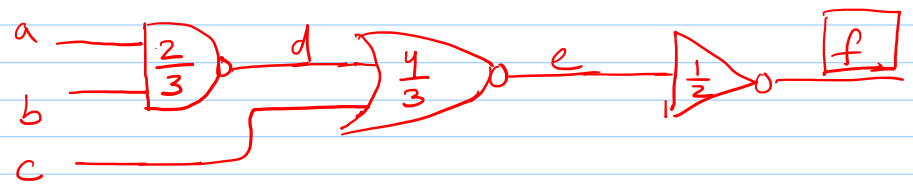Given $\left(\frac{\text{Rise delay}}{\text{fall delay}} \right)$ for each gate



$$\frac{\text{rise}}{\text{fall}} \text{ A.T. node "a"} = \frac{0}{0}$$

$$\text{" " " " "b"} = \frac{0}{0}$$

$$\text{" " " " "c"} = \frac{0}{0}$$

$$\text{R.T. at node "f"} = \frac{5}{11}$$

- (i) Find the R.T. at each node
- (ii) Find the slack at each node
- (iii) Critical path in the circuit

Node a A.T. = $\frac{0}{0}$ \leftarrow Rise A.T.
 $\frac{0}{0} \leftarrow$ Fall A.T.

$$\text{R.T.} = \frac{2}{-1}$$

$$\text{Slack} = \frac{2}{-1}$$

Node b A.T. = $\frac{0}{0}$

$$\text{R.T.} = \frac{5-3}{1-2} = \frac{2}{-1}$$

$$\text{Slack} = \frac{2}{-1}$$

o/p. R.T. fall = 5 ; fall delay (NAND) = 3
 o/p. R.T. rise = 1 ; rise delay (NAND) = 2



Node C : A.T. = 0

R.T. = $\frac{1}{5}$

Slack = $\frac{1-0}{5-0} = \frac{1}{5}$

Node d : A.T. = $\frac{2}{3}$ ← [i/p fall A.T. = 0 ; Rise delay = 2
i/p rise A.T. = 0 ; fall delay = 3

R.T. = $\frac{4-3}{9-4} = \frac{1}{5}$

Slack = $-\frac{1}{2}$


Node e : A.T. = $\frac{3+4}{2+3} = \frac{7}{5}$ ← [i/p fall A.T. = 3 ; Rise delay = 4
i/p rise A.T. = 2 ; Fall delay = 3

R.T. = $\frac{11-2}{5-1} = \frac{9}{4}$

[o/p fall R.T. = 11 ; fall delay = 2
o/p rise R.T. = 5 ; rise delay = 1

Slack = R.T. - A.T.
= $\frac{9-7}{4-5} = \frac{2}{-1}$

Slack = $\frac{2}{-1}$

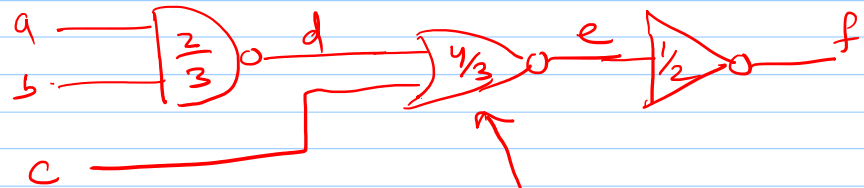



Node f

$$A.T. = \frac{5+1}{7+2} = \frac{6}{9} \quad \left\{ \begin{array}{l} \text{i/p. A.T. fall} = 5 ; \text{ Rise delay} = 1 \\ \text{i/p A.T. rise} = 7 \text{ fall delay} = 2 \end{array} \right.$$


$$\text{Given } R.T. = \frac{5}{11}$$
 
$$\text{Slack} = R.T. - A.T. = \frac{R.T.(\text{Rise}) - A.T.(\text{Rise})}{R.T.(\text{fall}) - A.T.(\text{fall})} = \frac{5-6}{11-9} = \frac{-1}{2}$$



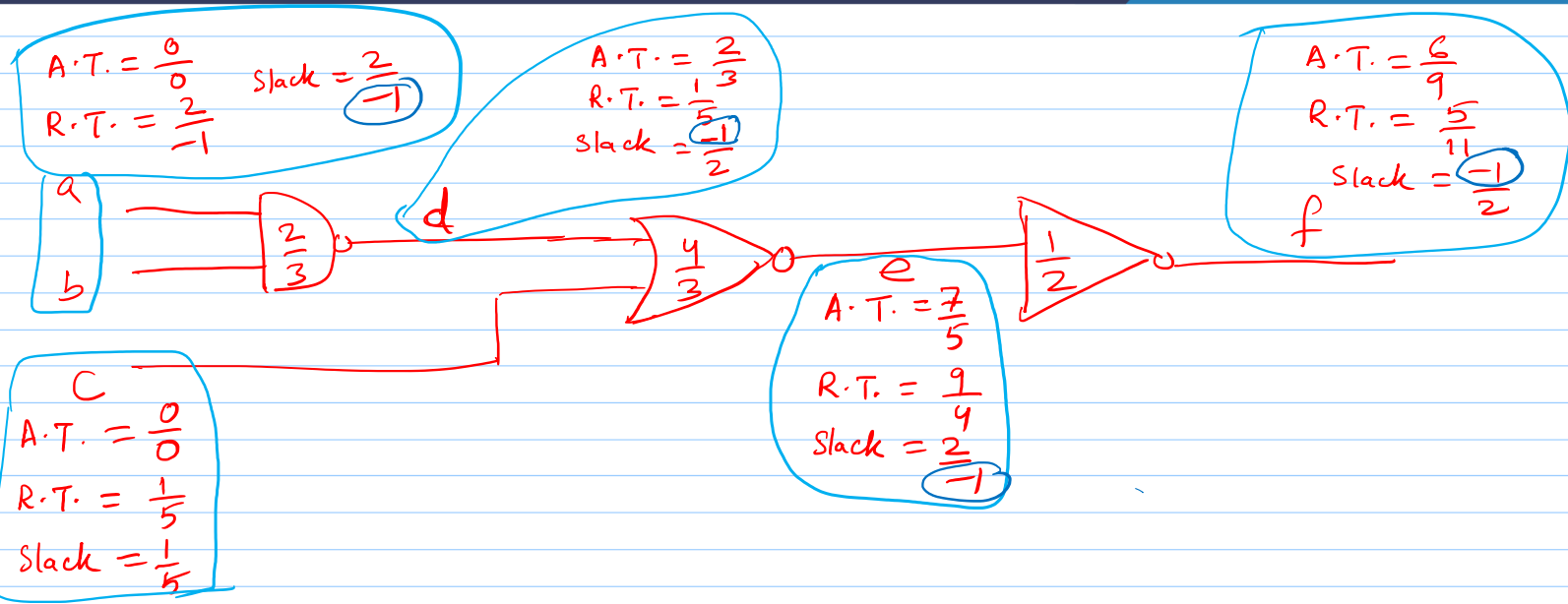

 "f" rising \rightarrow "e" falling \rightarrow "d" rising \rightarrow "a/b" falling



Thank You

