



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

VLSI Physical Design with Timing Analysis

Lecture – 7: Overview of Timing Analysis

Bishnu Prasad Das

Department of Electronics and Communication Engineering



Contents

- Timing Analysis
- Significance of Static Timing Analysis
- STA in VLSI Physical Design
- Static Timing Analysis
- Dynamic Timing Analysis
- Timing Paths





Timing Analysis

- Timing Analysis assesses and ensures that the designed circuit meets timing and performance requirements.
- Timing parameters of the circuit or chip, such as setup and hold times, clock-to-Q delays, and critical paths are evaluated and optimized.




Significance of Static Timing Analysis

  
- Determines the critical path of the design, which in turn determines the performance of the design.
- Determines the shortest path in the design (To avoid hold violation).
- Impact of **clock skew** and **clock jitter** on the timing of the design.
- Impact of **process variations** on the timing of the design.



STA in VLSI Physical Design

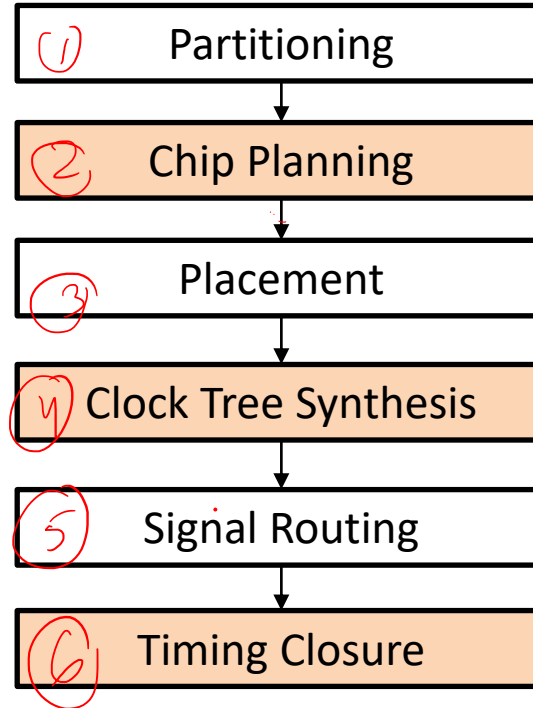

...

 



Timing Analysis

- Timing constraints for a chip are tested at a specified clock rate by employing either
 - Static Timing Analysis(STA) or
 - Dynamic Timing Analysis(DTA).



Static Timing Analysis(STA)

  - Checks static delay requirements of the circuit without applying input vectors or monitoring output vectors.
- Process of Static Timing Analysis:
 - Break a design down into timing paths.
 - Calculate the signal propagation delay along each path.
 - Check for violations of timing constraints inside the design and at the input/output interface.




Dynamic Timing Analysis(DTA)



- Verifies functionality of the design by applying input vectors and checking the outputs against expected outputs.
- Checks for logical correctness of the designed circuit.
- Simulation time is relatively more than STA as all inputs need to be checked.
- Best suitable for designs having clocks crossing multiple domains



Timing Paths

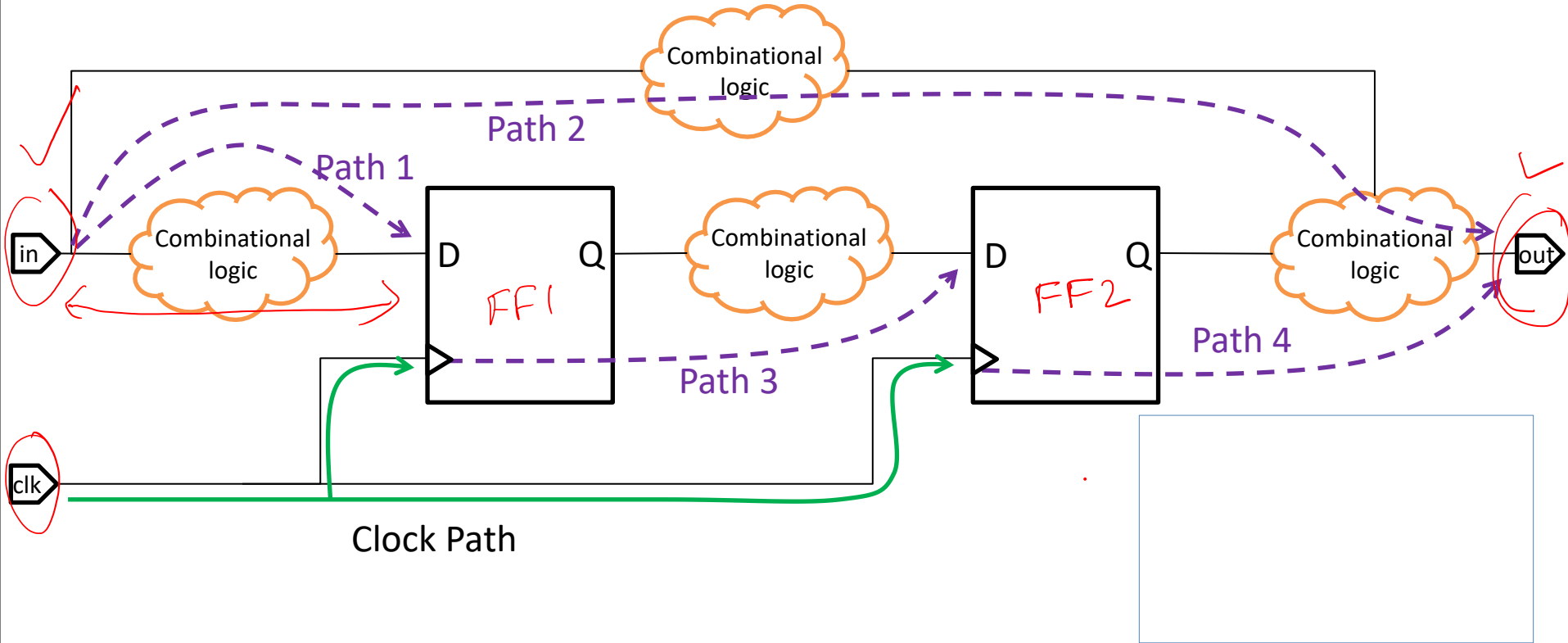


Timing Paths

 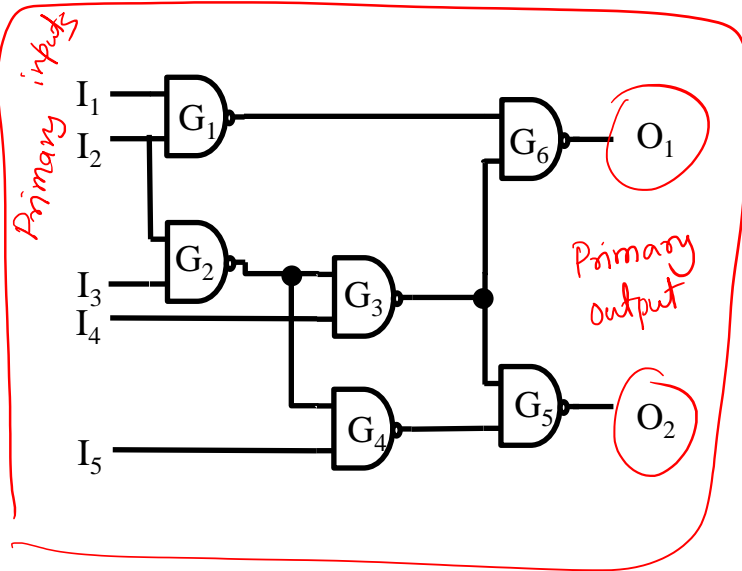

Directed Acyclic Graph
(DAG)

 Combinational Logic may have multiple paths



Timing Paths

- Critical Path: The path between an input and an output with the **maximum** delay.
- Shortest Path: The path between an input and an output with the **minimum** delay.





False Path

- A false path is **a path that exists in the design** which:
 1. is not functional; or
 2. is not required to meet its **timing constraints** for the design to function properly.



 
 
Example

- Let
 - Delay of the NOR gate = 4 ns
 - Delay of the MUX = 3 ns
 - Delay of the NOT gate = 1 ns
- Now, let's find the critical, shortest, and False paths in the given circuit.



 
 
Example

- Consider the given circuit
 - It has five paths
 - P1: NOR + MUX
 - P2: NOR + MUX + NOR + MUX
 - P3: NOR + MUX + MUX
 - P4: NOT + MUX + NOR + MUX
 - P5: NOT + MUX + MUX





  Example

- Delay of P1 = NOR + MUX
= 4 + 3
= 7 ns
- Delay of P2 = NOR + MUX + NOR + MUX
= 4 + 3 + 4 + 3
= 14 ns
- Delay of P3 = NOR + MUX + MUX
= 4 + 3 + 3
= 10 ns






  - Delay of P4 = NOT + MUX + NOR + MUX
 $= 1 + 3 + 4 + 3$
 $= 11 \text{ ns}$
- Delay of P5 = NOT + MUX + MUX
 $= 1 + 3 + 3$
 $= 7 \text{ ns}$



   Example

- Delay of P1 = 7 ns
- Delay of P2 = 14 ns
- Delay of P3 = 10 ns
- Delay of P4 = 11 ns
- Delay of P5 = 7ns



Example

- Critical Path:



- **Case – 1:** $T = 0$

- Delay of P3 = NOR + MUX + MUX
 $= 4 + 3 + 3$
 $= 10 \text{ ns}$

- **Case – 2:** $T = 1$

- Delay of P4 = NOT + MUX + NOR + MUX
 $= 1 + 3 + 4 + 3$
 $= 11 \text{ ns}$

Critical path delay

  

Thank You

